

Tutorial-1: Communication Circuit Design


L3 - Semiconductors and PN Junction

Question 3.1: Determine whether each silicon diode in Figure below is forward-biased or reverse-biased.

Question 3.2: Determine the voltage across each diode in Figure below, assuming the practical model.

Question 3.3: Determine the voltage across each diode in Figure below, assuming an ideal diode.

Question 3.4: Determine the voltage across each diode in Figure below, using the complete diode model with $r'_d = 10\ \Omega$ and $r'_R = 100\ \text{M}\Omega$

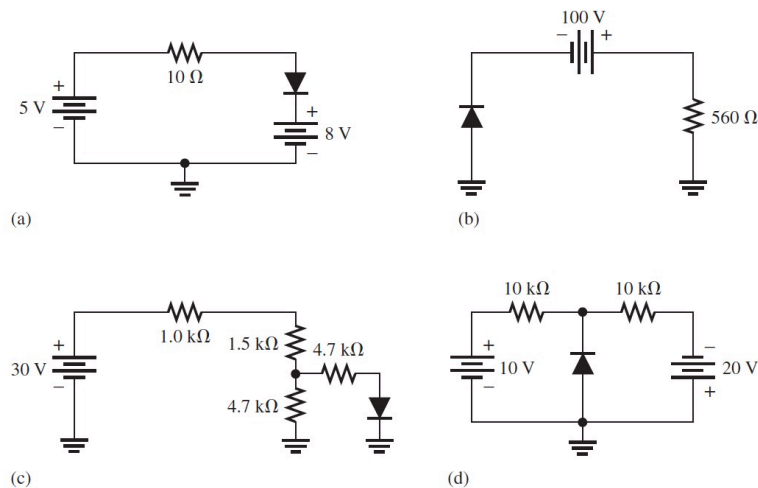

Answer 3.1:

- (a) The diode is reverse-biased.
- (b) The diode is forward-biased.
- (c) The diode is forward-biased.
- (d) The diode is forward-biased.

Answer 3.2:

- (a) $V_R = 5\ \text{V} - 8\ \text{V} = -3\ \text{V}$
- (b) $V_F = 0.7\ \text{V}$
- (c) $V_F = 0.7\ \text{V}$
- (d) $V_F = 0.7\ \text{V}$

Answer 3.3:

- (a) $V_R = 5\ \text{V} - 8\ \text{V} = -3\ \text{V}$
- (b) $V_F = 0\ \text{V}$
- (c) $V_F = 0\ \text{V}$
- (d) $V_F = 0\ \text{V}$

Answer 3.4:Ignoring r'_R :

$$(a) \quad V_R \cong 5 \text{ V} - 8 \text{ V} = \mathbf{-3 \text{ V}}$$

$$(b) \quad I_F = \frac{100 \text{ V} - 0.7 \text{ V}}{560 \, \Omega + 10 \, \Omega} = 174 \text{ mA}$$

$$V_F = I_F r'_d + V_B = (174 \text{ mA})(10 \, \Omega) + 0.7 \text{ V} = \mathbf{2.44 \text{ V}}$$

$$(c) \quad I_{tot} = \frac{30 \text{ V}}{R_{tot}} = \frac{30 \text{ V}}{4.85 \text{ k}\Omega} = 6.19 \text{ mA}$$

$$I_F = \frac{6.19 \text{ mA}}{2} = 3.1 \text{ mA}$$

$$V_F = I_F r'_d + 0.7 \text{ V} = (3.1 \text{ mA})(10 \, \Omega) + 0.7 \text{ V} = \mathbf{0.731 \text{ V}}$$

(d) Approximately all of the current from the 20 V source is through the diode. No current from the 10 V source is through the diode.

$$I_F = \frac{20 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega + 10 \, \Omega} = 1.92 \text{ mA}$$

$$V_F = (1.92 \text{ mA})(10 \, \Omega) + 0.7 \text{ V} = \mathbf{0.719 \text{ V}}$$


L4 - Bipolar Junction Transistor (BJT)

Question 4.1: A certain transistor has an $I_C = 25 \text{ mA}$ and an $I_B = 200 \text{ }\mu\text{A}$. Determine the β_{DC} .

Question 4.2: What is the β_{DC} of a transistor if $I_C = 20.3 \text{ mA}$ and $I_E = 20.5 \text{ mA}$.


Question 4.3: What is the α_{DC} if $I_C = 5.35 \text{ mA}$ and $I_B = 50 \text{ }\mu\text{A}$?

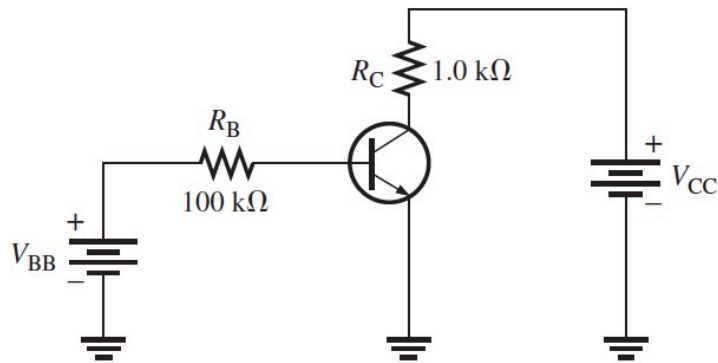Question 4.4: A base current of $50 \text{ }\mu\text{A}$ is applied to the transistor in Figure below, and a voltage of 5 V is dropped across R_C . Determine the β_{DC} of the transistor.




Question 4.5: Assume that the transistor in the circuit of Figure above is replaced with one having a β_{DC} of 200. Determine I_B , I_C , I_E , and V_{CE} given that $V_{CC} = 10 \text{ V}$ and $V_{BB} = 3 \text{ V}$.

Question 4.6: Determine each current in Figure below. What is the β_{DC} ?

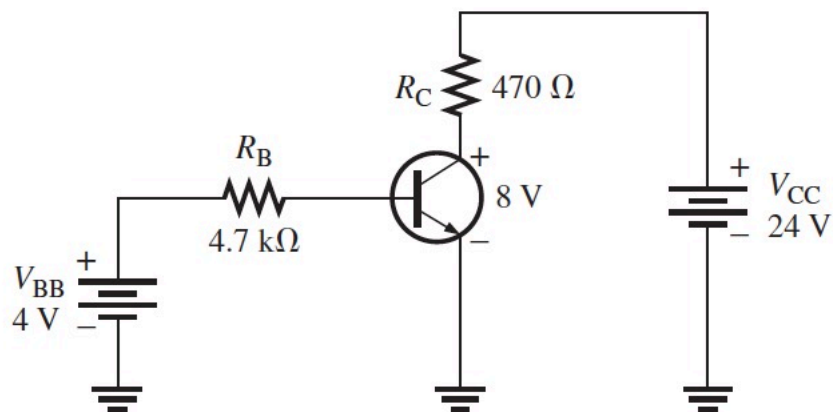

Question 4.7: Find V_{CE} , V_{BE} , and V_{CB} in the circuits of Figure below.

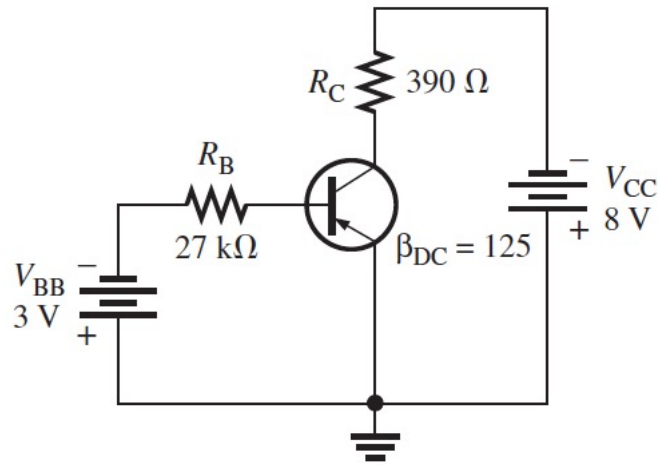

Answer 4.1:

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{25 \text{ mA}}{200 \mu\text{A}} = \mathbf{125}$$

Answer 4.2:

$$I_B = I_E - I_C = 20.5 \text{ mA} - 20.3 \text{ mA} = 0.2 \text{ mA} = 200 \mu\text{A}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{20.3 \text{ mA}}{200 \mu\text{A}} = \mathbf{101.5}$$

Answer 4.3:

$$I_E = I_C + I_B = 5.35 \text{ mA} + 50 \mu\text{A} = 5.40 \text{ mA}$$

$$\alpha_{DC} = \frac{I_C}{I_E} = \frac{5.35 \text{ mA}}{5.40 \text{ mA}} = \mathbf{0.99}$$

Answer 4.4:

$$I_C = \frac{V_{R_C}}{R_C} = \frac{5 \text{ V}}{1.0 \text{ k}\Omega} = 5 \text{ mA}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{5 \text{ mA}}{50 \mu\text{A}} = \mathbf{100}$$

Answer 4.5:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = \mathbf{23 \mu A}$$

$$I_C = \beta_{DC} I_B = 200(23 \mu A) = \mathbf{4.6 \text{ mA}}$$

$$I_E = I_C + I_B = 4.6 \text{ mA} + 23 \mu A = \mathbf{4.62 \text{ mA}}$$

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (4.6 \text{ mA})(1.0 \text{ k}\Omega) = \mathbf{5.4 \text{ V}}$$

Answer 4.6:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4 \text{ V} - 0.7 \text{ V}}{4.7 \text{ k}\Omega} = \frac{3.3 \text{ V}}{4.7 \text{ k}\Omega} = \mathbf{702 \mu A}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{24 \text{ V} - 8 \text{ V}}{470 \Omega} = \mathbf{34 \text{ mA}}$$

$$I_E = I_C + I_B = 34 \text{ mA} + 702 \mu A = \mathbf{34.7 \text{ mA}}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{34 \text{ mA}}{702 \mu A} = \mathbf{48.4}$$

Answer 4.7:

$$V_{BE} = \mathbf{-0.7 \text{ V}}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{-3 \text{ V} - (-0.7 \text{ V})}{27 \text{ k}\Omega} = \frac{-2.3 \text{ V}}{27 \text{ k}\Omega} = \mathbf{-85.2 \mu A}$$

$$I_C = \beta_{DC} I_B = 125(-85.2 \mu A) = \mathbf{-10.7 \text{ mA}}$$

$$V_{CE} = V_{CC} - I_C R_C = -8 \text{ V} - (-10.7 \text{ mA})(390 \Omega) = \mathbf{-3.83 \text{ V}}$$

$$V_{CB} = V_{CE} - V_{BE} = -3.83 \text{ V} - (-0.7 \text{ V}) = \mathbf{-3.13 \text{ V}}$$

L5 - Field-Effect Transistor (FET)

Question 5.1:

A JFET has a specified pinch-off voltage of 5 V. When $V_{GS} = 0$, what is V_{DS} at the point where the drain current becomes constant?

Question 5.2:


A certain n -channel JFET is biased such that $V_{GS(off)} = -2$ V. What is the value of $V_{GS(off)}$ if V_P is specified to be 6 V? Is the device on?

Question 5.3:

A certain JFET datasheet gives When $V_{GS(off)} = -8$ V and $I_{DSS} = 10$ mA. When $V_{GS} = 0$, what is I_D for values of V_{DS} above pinch off? $V_{DD} = 15$ V.

Question 5.4:

The JFET in Figure below has a $V_{GS(off)} = -4$ V. Assume that you increase the supply voltage, V_{DD} , beginning at zero until the ammeter reaches a steady value. What does the voltmeter read at this point?

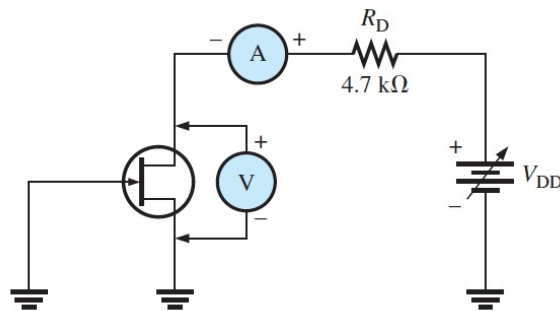

Question 5.5:


For a particular JFET, $g_{m0} = 3200$ μS . What is g_m when $V_{GS} = -4$ V given that $V_{GS(off)} = -8$ V?

Question 5.6:


A p -channel JFET datasheet shows that $I_{GSS} = 5$ nA at $V_{GS} = 10$ V. Determine the input resistance.

Question 5.7:


For each circuit in Figure below, determine V_{DS} and V_{GS} .

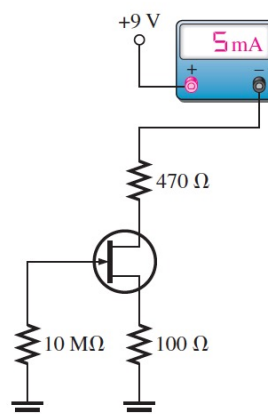

Question 5.8: Using the curve in Figure below, determine the value of R_S required for a 9.5 mA drain current.

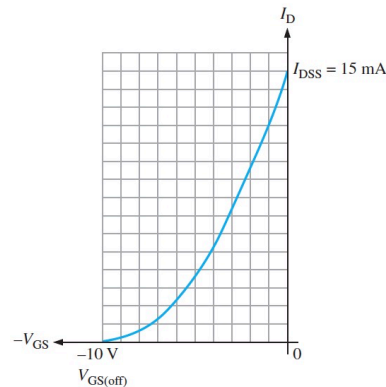

Question 5.9: Graphically determine the Q-point for the circuit in Figure (a) below using the transfer characteristic curve in Figure (b).

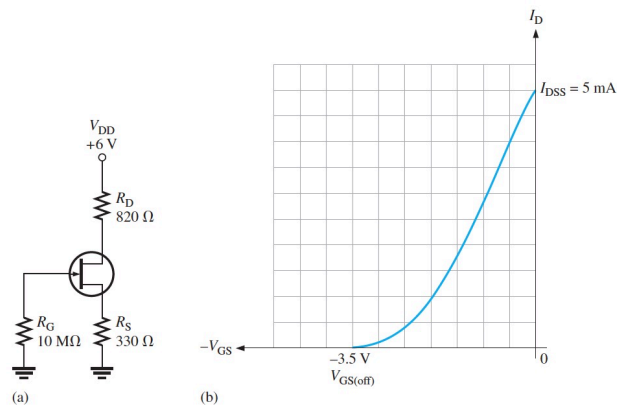

Question 5.10: The Q-point of a JFET is varied from $V_{DS} = 0.4$ V and $I_D = 0.15$ mA to $V_{DS} = 0.6$ V and $I_D = 0.45$ mA. Determine the range of R_{DS} values.

Answer 5.1:

$V_{DS} = V_P = 5$ V at point where I_D becomes constant.

Answer 5.2:

$$V_{GS(off)} = -V_P = -6 \text{ V}$$

The device is **on**, because $V_{GS} = -2$ V.

Answer 5.3:

By definition, $I_D = I_{DSS}$ when $V_{GS} = 0$ V for values of $V_{DS} > V_P$.
Therefore, $I_D = \mathbf{10\text{ mA}}$.

Answer 5.4:

$$V_P = -V_{GS(off)} = -(-4\text{ V}) = 4\text{ V}$$

The voltmeter reads V_{DS} . As V_{DD} is increased, V_{DS} also increases. The point at which I_D reaches a constant value is $V_{DS} = V_P = \mathbf{4\text{ V}}$.

Answer 5.5:

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right) = 3200\text{ }\mu\text{S} \left(1 - \frac{-4\text{ V}}{-8\text{ V}} \right) = \mathbf{1600\text{ }\mu\text{S}}$$

Answer 5.6:

$$R_{IN} = \frac{V_{GS}}{I_{GSS}} = \frac{10\text{ V}}{5\text{ nA}} = \mathbf{2000\text{ M}\Omega}$$

Answer 5.7:

$$V_S = (5\text{ mA})(100\text{ }\Omega) = 0.5\text{ V}$$

$$V_D = 9\text{ V} - (5\text{ mA})(470\text{ }\Omega) = 6.65\text{ V}$$

$$V_G = 0\text{ V}$$

$$V_{GS} = V_G - V_S = 0\text{ V} - 0.5\text{ V} = \mathbf{-0.5\text{ V}}$$

$$V_{DS} = 6.65\text{ V} - 0.5\text{ V} = \mathbf{6.15\text{ V}}$$

Answer 5.8:

From the graph, $V_{GS} \cong -2\text{ V}$ at $I_D = 9.5\text{ mA}$.

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \left| \frac{-2\text{ V}}{9.5\text{ mA}} \right| = \mathbf{211\text{ }\Omega}$$

Answer 5.9:

For $I_D = 0$,

$$V_{GS} = -I_D R_S = (0)(330\text{ }\Omega) = 0\text{ V}$$

For $I_D = I_{DSS} = 5\text{ mA}$

$$V_{GS} = -I_D R_S = -(5\text{ mA})(330\text{ }\Omega) = -1.65\text{ V}$$

From the graph in Figure 8-69 in the textbook, the Q -point is

$$V_{GS} \cong \mathbf{-0.95\text{ V}} \text{ and } I_D \cong \mathbf{2.9\text{ mA}}$$

Answer 5.10:

$$R_{DS1} = \frac{0.4 \text{ V}}{0.15 \text{ mA}} = 2.67 \text{ k}\Omega$$

$$R_{DS2} = \frac{0.6 \text{ V}}{0.45 \text{ mA}} = 1.33 \text{ k}\Omega$$

$$\Delta R_{DS} = 2.67 \text{ k}\Omega - 1.33 \text{ k}\Omega = \mathbf{1.34 \text{ k}\Omega}$$